

**INDIAN INSTITUTE OF TECHNOLOGY BOMBAY**  
**ELECTRICAL ENGINEERING DEPARTMENT**  
**EE-Midsem**

Monday Apr. 24, 2023 Time: 15:15-16:00	MS-101 Makerspace Spring Semester 2022-23	Marks: 40 (To be re-scaled)
---	--	--------------------------------

Roll Number: \_\_\_\_\_ Name: \_\_\_\_\_

Division: \_\_\_\_\_ Batch: \_\_\_\_\_ Signature: \_\_\_\_\_

Answer the following in the space provided with the questions.

**Q-1** Circuit diagram of the op amp I to V converter used in Expt. 3 is shown below.


The device under test (DUT) is connected between terminals B and C.

Assume that the op amp is ideal.

$+V_{cc} = +12\text{ V}$ ,  $-V_{cc} = -12\text{ V}$ ;  $R_1 = 1\text{ k}\Omega$ ,  $R_F = 2\text{ k}\Omega$ .

Also assume that the maximum and minimum  $V_{Out}$  levels are  $+V_{cc}$  and  $-V_{cc}$  respectively. Calculation steps must be shown with your answer.

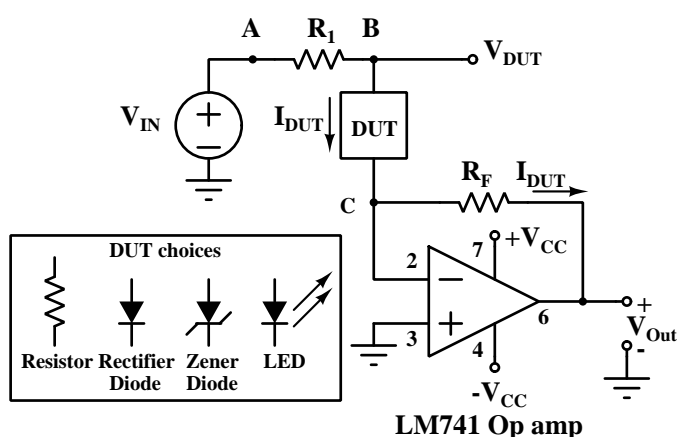**No marks will be awarded without proper steps.**



a) A  $1\text{ k}\Omega$  resistor is connected as the DUT.

<p>If <math>V_{IN} = +4\text{ V}</math>, what will be the values of <math>V_{DUT}</math> and <math>V_{Out}</math>?</p> <p>Answer:</p>	<p><b>Steps:</b> <math>R_1 = R = 1\text{ k}\Omega</math>          (connected between <math>4\text{ V}</math> and virtual ground).          So <math>V_{DUT} = 2\text{ V}</math>. (Pot. division bet. <math>R_1</math> and <math>R</math>).  <math>I_{DUT} = V_{DUT}/R = 2\text{ V}/1000\Omega = 2\text{ mA}</math>.  <math>V_{out} = -2\text{ mA} * R_F = -2\text{ mA} * 2\text{ k} = -4\text{ V}</math></p> <div style="display: flex; align-items: center;"> <div style="border: 1px solid black; padding: 2px; margin-right: 10px;"> <math>V_{DUT} = \underline{2.0\text{ V}}</math> </div> <div style="border: 1px solid black; padding: 2px; margin-right: 10px;"> <math>V_{Out} = \underline{-4.0\text{ V}}</math> </div> <div>0.5 mark penalty for wrong sign</div> </div>
---	---

- [2]

b) a Zener diode is connected as the DUT with its anode at terminal B and cathode at terminal C. The Zener voltage is  $3.2\text{ V}$ , and the Zener I-V characteristic is linear in the Zener region with a slope of  $200\text{ }\Omega$ .

<p>If <math>V_{IN} = -8</math> V, what will be the values of <math>V_{DUT}</math> and <math>I_{DUT}</math>?</p> <p>Answer:</p>	<p><b>Steps:</b> For applied voltage <math>&gt;</math> Zener voltage,  <math>I_{DUT} = -(8 - 3.2)/(1000 + 200) = -4.8/1200 = -4.0</math> mA.  <math>V_{DUT} = -(200 *  I_{DUT}  + 3.2) = -(0.8 + 3.2) = -4.0</math> V.</p> <div style="display: flex; justify-content: space-around; align-items: center;"> <div style="border: 1px solid black; padding: 2px 10px;"><math>V_{DUT} = \underline{-4.0\text{V}}</math></div> <div style="border: 1px solid black; padding: 2px 10px;"><math>I_{DUT} = \underline{-4.0\text{mA}}</math></div> </div> <p>0.5 mark penalty for wrong sign</p>
--	--

– [2]


- c) an LED is connected as the DUT with its anode at terminal B and cathode at terminal C. The LED cut-in voltage is 2.5 V (below this voltage the LED draws negligible current).

<p>If <math>V_{IN} = +2</math> V, what will be the values of <math>V_{DUT}</math> and <math>V_{Out}</math>?</p> <p>Answer:</p>	<p><b>Steps:</b> No current through the LED since the voltage is less than cut in voltage. So Op amp output is 0 V, and there is no drop across the current limiter resistor <math>R_1</math>.</p> <div style="display: flex; justify-content: space-around; align-items: center;"> <div style="border: 1px solid black; padding: 2px 10px;"><math>V_{DUT} = \underline{2.0\text{ V}}</math></div> <div style="border: 1px solid black; padding: 2px 10px;"><math>V_{Out} = \underline{0.0\text{ V}}</math></div> </div> <p>0.5 mark penalty for wrong sign</p>
--	---

– [2]

– [Q1: 2+2+2=6 marks]

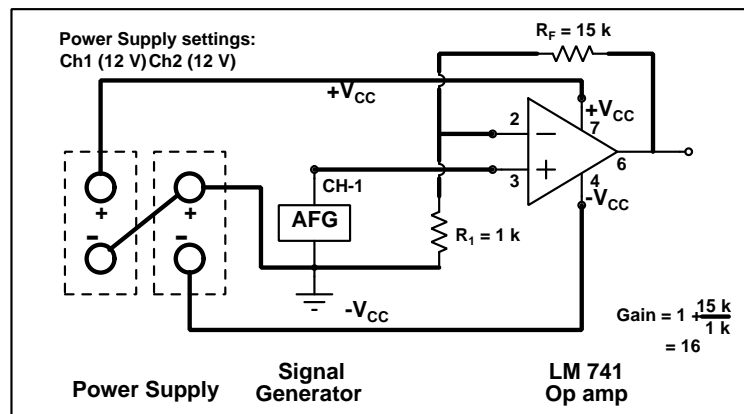**Q–2** Three blocks with their terminals, *viz.* Power supply, AFG and LM 741 op amp are shown below.



Show the wiring between these three blocks so as to obtain a **non-inverting** amplifier with a voltage gain of **16**. (Add the connections to the diagram above).

Connect also the required resistors out of the following resistor values:

1 k $\Omega$ , 10 k $\Omega$ , 15 k $\Omega$ , 16 k $\Omega$ , 17 k $\Omega$ , 160 k $\Omega$  and 170 k $\Omega$ .

Assume that both Ch1 and Ch2 of Power supply are set at 12 V. You must use the Power supply Ch1 as  $+V_{CC}$  and Ch2 as  $-V_{CC}$ .

– [Q2: 5 marks]

### Marking Key for Q2:

Ch1 +	to Opamp $+V_{CC}$	0.5
Ch1 -	to Ch2 + and Ground	$0.5+0.5 = 1.0$
Ch2 -	to Opamp $-V_{CC}$	0.5
AFG top	to Opamp non-inv (3)	0.5
Opamp out(6)	to Inv input (2) through $R_F$	0.5
Opamp Inv (2)	to Ground through $R_1$	0.5
Opamp config	for non inverting amp	0.5
Choices of R	$R_F$ and $R_1$ values	1.0

**Q-3** A digital circuit receives a natural number in the range  $0 \leq n \leq 15$  represented by 4 bits ABCD (with A as the most significant bit). We want to design the logic for outputting a ‘Select’ signal when  $n$  is any one of 0, 1, 2, 8, 9 or 10.

a)

Fill entries in the truth table shown on the right for ‘Select’ as a function of A, B, C and D. **Be very careful with these entries. Errors in this part will lead to wrong results in the remaining parts!**

Answer:

A	B	C	D	Select
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

0.5 mark penalty for every wrong entry

– [2]

b)

Express ‘select’ in canonical form as a sum of products.

Answer:

$$\overline{A} \overline{B} \overline{C} \overline{D} + \overline{A} \overline{B} \overline{C} D + \overline{A} \overline{B} C \overline{D} + A \overline{B} \overline{C} \overline{D} + A \overline{B} \overline{C} D + A \overline{B} C \overline{D}$$


0.5 mark penalty for every wrong entry

– [2]

c)

Fill entries in the Karnaugh map shown on the right for 'Select' as a function of A, B, C and D.

 Show the maximal groupings of '1's in the Karnaugh map above and derive the **minimal** logic expression for 'select' in terms of A,B,C,D and their complements.



$$\text{Select} = \bar{B} \bar{D} + \bar{B} \bar{C} + B C + B D$$

$$\text{Select} = \bar{B} \cdot (\bar{C} + \bar{D})$$

2 marks for the correct minimized expression.

(if only one term is correct, then 1 mark)

0.5 mark penalty for every wrong entry

1 mark for correct K map.  
1 mark for correct circlings

– [4]


– Q3: 2+2+4 = 8 marks

Q-4

We need to generate the function:  
 $f = (\bar{P} + \bar{Q}) \cdot (\bar{R} + \bar{S})$  from input signals  $P, Q, R$  and  $S$ . (Their complements are not provided as inputs).

IC 7400 provides 4 2-input NAND gates in a single package. Implement the function  $f$  using a single 7400 package (*i.e.* Using 4 or fewer 2-input NAND gates).

Logic Diagram:

 

Partial marks only if the first two gates (P, Q, R, S) are correctly connected.


Correct P, Q, R, S connection: 2 marks

Correct connections of the third NAND gate: 2 marks

– Q4: 5 marks

Q-5

 Consider the circuit on the right using two positive edge triggered JK flipflops. You are given that at  $t=0$ ,  $Q1 = Q2 = 0$ .



Four positive clock edges arrive after this initial state. What will be values of Q1 and Q2 after the arrival of each of the clock edges?

	Q1	Q2
At $t=0$	0	0
After Clock1	1	0
After Clock2	1	1
After Clock3	1	0
After Clock4	1	1

No marks if 'After Clock 1' Q1 and Q2 are wrong.

1 mark penalty for every wrong entry from Clock2 onwards

– Q5: 4 marks

Q-6 a) What is the least number of bits required to represent:

- 128 (decimal) in unsigned binary format,
- +128 (decimal) in two's complement signed format,
- 128 (decimal) in two's complement signed format,
- +15 (decimal) in two's complement signed format.

Answer: 8

Answer: 9

Answer: 8

Answer: 5

– [2]

b) i) Represent the unsigned number 1123 (decimal) in base 16 format (Hex code) as a 12 bit wide quantity.

Answer: 463 in Hex

ii) Represent the same number (1123 decimal) in base 8 format (octal) as a 12 bit wide quantity.

Answer: 2143 in octal

– [2]

c) What decimal signed number is represented by the 12 bit Hex number D28 if we are using 2's complement convention for signed numbers?


Answer: -728


– [1]

– [Q6: 2 + 2 + 1 = 5 marks]

Q-7

 Outputs of two **open collector** buffer gates are shorted as shown in the logic diagram on the right. Waveforms for the inputs applied to the two gates are shown below.




 

2 marks penalty for every wrong pulse.

Add the waveform at the terminal marked Out to the figure with the same time scale as In1 and In2. – [Q7: 5marks]

Q-8

 

Find the voltage at nodes A and B in the circuit shown on the left. The voltage source provides 4V.

Voltage at node A is: 2 V

Voltage at node B is: 1 V

– [Q8: 2 marks]

**Paper Ends**

Rough Work