

Lect 1,2,3: Sample Questions

Practice Problems – Set 1 (April 2, 2023)

1. How would you define (in words) an ideal current source? Sketch its I-V characteristics.
2. Out of the following devices, choose ALL the ones which are single-port devices
 - a. Resistor
 - b. Transformer
 - c. Inductor
 - d. Bipolar Junction Transistor
 - e. Capacitor
3. A *pn* junction diode has the following parameters: $I_S = 10^{-15}$ A, $V_T = (kT/q) = 25$ mV. Determine the current I_D through the diode for the following diode voltages V_D :
i) $V_D = 0.2$ V, ii) $V_D = 0.5$ V, iii) $V_D = 0.7$ V, iv) $V_D = 0.8$ V, and $V_D = -1$ V.
4. Sketch the I-V characteristics of a silicon *pn* junction diode. You may assume the diode to be similar to the one you used in EE Expt 2 of the MS101 lab ($I_S = 10^{-14}$ A, $V_T = (kT/q) = 25$ mV). Mark the salient points, i.e. the typical voltages and currents.
5. A few statements are given below. For each statement, specify whether it is TRUE or FALSE.
 - a) The light emitted by an LED is inversely proportional to the current flowing through it.
 - b) A Solar cell requires an external bias voltage for its operation.
 - c) An optocoupler is a combination of an LED and a photodiode and is used for passing on signal from one end to another with electrical isolation between them.
6. Sketch the circuit diagram of a half-wave rectifier with a capacitive filter. Sketch also the typical V_{out} waveform. What will be the effect of decreasing the capacitor on the ripple voltage in V_{out} ? Justify your answer.
7. What are line and load regulations applied to a DC power supply?
8. In experiment 2, which DC power supply - the bridge rectifier with a capacitor filter of $1000\ \mu\text{F}$ or the 7805 IC regulator – had lower output resistance? Justify your answer.